

The DLX713X, 5x7 Dot Matrix Intelligent Display[®] Device Appnote 25


This application note is intended to serve as a design and application guide for users of the DLO7135 and DLG7137 OSRAM Intelligent Displays. This appnote covers device electrical description, operation, general circuit design considerations and interfacing to microprocessors.

Electrical Description

The DLX713X intelligent alphanumeric 5x7 dot matrix display contains memory, character generator, multiplexing circuits, and drivers built into a single package.

Figure 1 is a block diagram of the DLX713X. The unit consists of 35 LED die arranged in a 5x7 pattern and a single CMOS integrated circuit chip. The IC chip contains the column drivers, row drivers, 128 character generator ROM, memory, multiplex and blanking circuitry.

Figure 1. DLX713X block diagram

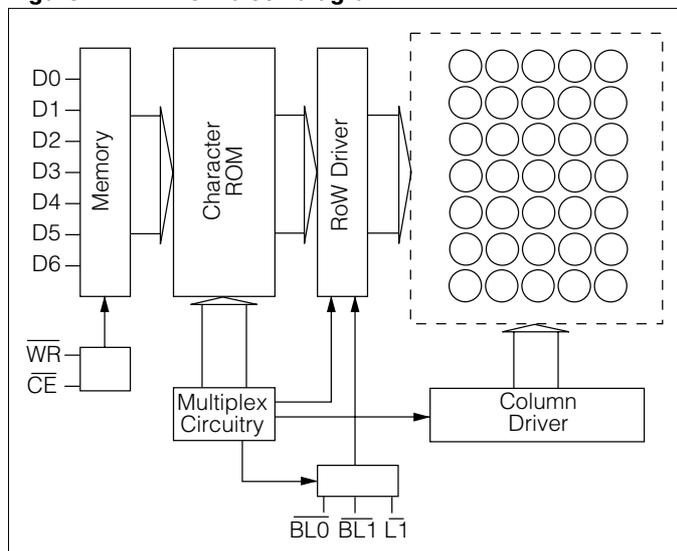

Package

Thirty-five dots form a 0.48 x 0.68 inch overall dot size. The display is housed in a 0.700 x 0.800 inch dual-in-line package. The $\pm 5^\circ$ viewing angle complements the large display area. The display is a filled reflector type with the integrated circuit in a filled with IC-grade epoxy. This results in a very robust package which is resistant to moisture, shock, and vibration.

Figure 2. Physical dimensions in inches (mm)

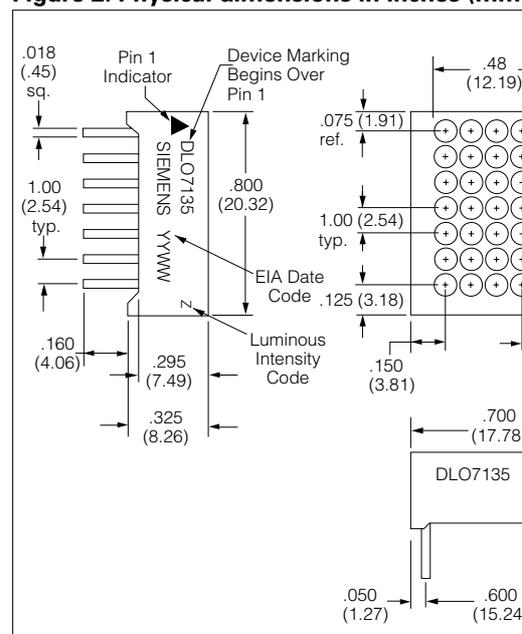


Table 1. Electrical inputs

Pin	Name	Pin	Name
1	V _{CC}	14	D6 data input (MSD)
2	$\overline{\text{LT}}$ lamp test	13	D5 data input
3	$\overline{\text{CE}}$ chip enable	12	D4 data input
4	$\overline{\text{WR}}$ write	11	D3 data input
5	$\overline{\text{BL1}}$ brightness	10	D2 data input
6	$\overline{\text{BL0}}$ brightness	9	D1 data input
7	GND	8	D0 data input (LSD)

Table 2. Pin description

V _{CC}	Positive Supply +5 V
GND	Ground
D0–D6	Data Lines, see Figure 3 (Character set)
$\overline{\text{CE}}$	Chip Enable (active low) Determines which device in an array will accept data
$\overline{\text{WR}}$	Write (active low) Data and chip enable must be present and stable before and after the write pulse (see DLX713X data sheet for timing)
$\overline{\text{BL0}}, \overline{\text{BL1}}$	Blanking Control Input (active low) Used to control level of display brightness
$\overline{\text{LT}}$	Lamp Test (active low) Causes all dots to light at 1/2 brightness

Operation

In a dot matrix display system, it is advantageous to use a multiplexed approach with 12 drivers (5 digit plus 7 segments) rather than 35 segment drivers, reducing the number of drives and interconnections required. A multiplexed system must be a synchronous system or the digits or elements may have different on (lit) times and therefore varying brightness.

The DLX713X is an internally multiplexed display but the data entry is asynchronous. Loading data is similar to writing into a RAM. Present the data, select the chip, and give a write signal. For a multidigit system, each digit has its own unique location and will display its contents until replaced by another code.


The waveforms of Figure 4 demonstrates the relationship of the signals required to generate a write cycle. Check the data sheet for minimum values required for each signal.

Figure 3. Character set

ASCII CODE	D0	D1	D2	D3	D4	D5	D6	HEX	0	1	2	3	4	5	6	7	8	9	A	B
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	2	2	2	2	2	2	0	0	0	0	0	0	0	0	0	0	0	0
0	1	1	3	3	3	3	3	3	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	4	4	4	4	4	4	0	0	0	0	0	0	0	0	0	0	0	0
1	0	1	5	5	5	5	5	5	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	6	6	6	6	6	6	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	7	7	7	7	7	7	0	0	0	0	0	0	0	0	0	0	0	0

1. High=1 level. 2. Low=0 level.

Figure 4. Timing characteristics

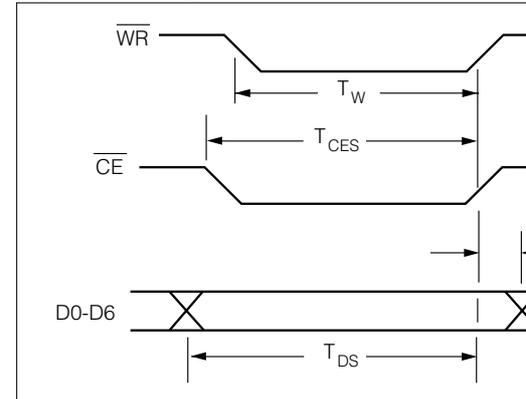

Display Blanking and Dimming

The DLX713x Intelligent Display has the capability of different levels of brightness plus blank. Figure 5 shows the relationship of $\overline{\text{BL0}}$ and $\overline{\text{BL1}}$ for the different levels of brightness. The $\overline{\text{BL0}}$ and $\overline{\text{BL1}}$ inputs are independent of write and does not affect the contents of the internal RAM. Flashing display can be achieved by pulsing the $\overline{\text{BL0}}$ or $\overline{\text{BL1}}$ at a 1–2 hertz rate. Either $\overline{\text{BL0}}$ or $\overline{\text{BL1}}$ should be used to light up the display.

Table 3. Dimming and blanking control

Brightness Level	$\overline{\text{BL1}}$
Blank	0
1/7 brightness	0
1/2 brightness	1
full brightness	1

Lamp Test

The lamp test when activated causes all dots on the display to be illuminated at 1/7 brightness. It does not destroy any previously stored characters. The lamp test function is independent of chip enable, write, and the settings of the blanking inputs.

This convenient test gives a visual indication that all dots are functioning properly. Because lamp test does not affect the display memory, it can be used as a cursor or pointer in a line of displays.

General Design Considerations

When using the DLX713X on a separate display board having more than six inches of cable length, it may be necessary to buffer all of the input lines. A non-inverting 74LS244 buffer can be used. The object is to prevent transient current into the DLX713x protection diodes. The buffers should be located on the display board and as close to the displays as possible.

Because of high switching currents caused by the multiplexing, local power supply bypass capacitors are also needed in many cases. These should be 10 volt, tantalum type having 10 uf capacitance. The capacitors may only be required every 2 displays depending on the line regulation and other noise generators.

Decoupling capacitors should also be used across V_{CC} and ground of each display. Typical value of these capacitors is 0.01 mF/10 V.


If small wire cables are used it is good engineering practice to calculate the wire resistance of the ground and the +5 volt wires. More than 0.2 volt drop (at 100 ma per digit) should be avoided, since this loss is in addition to any inaccuracies or load regulation of the power supply.

The 5 volt power supply for the DLX713X should be the same one supplying the V_{CC} to all logic devices. If a separate supply must be used then local buffers should be used on all the inputs and these buffers should be powered from the display power supply. This precaution is to avoid line transients or any logic signals to be higher than V_{CC} during power up.

Interfacing

For an eight digit display using the DLX713X, interfacing a single chip microprocessor is easy and straight forward.

Figure 5. Block diagram of the Intel 8031 connected to the DLX713X.

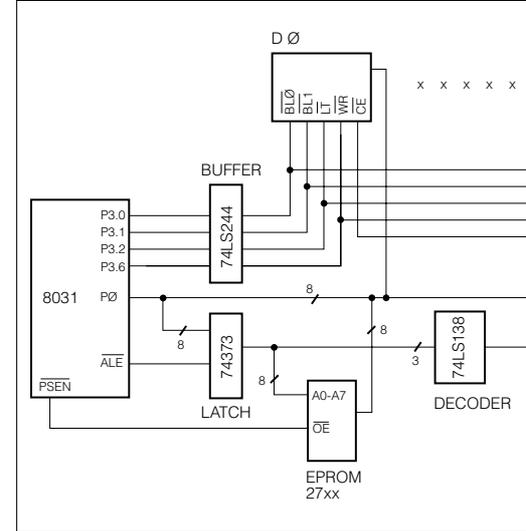

Conclusion

Note that although other manufacturers' products are shown in the examples, this application note does not imply endorsement, or warranty of other manufacturers' products. The interface schemes shown demonstrate the simplicity of using the DLX713X dot matrix Intelligent Display. Timing differences may be encountered for various applications, but can be resolved similar to those encountered when using different RAM's. The techniques used in this note were shown for their generality. The user will need to use other schemes to optimize his particular system requirements.

Program Listing

```

1          ; BY DAN WATSON
2          ; TO DO LAMP TEST,SET 100% BRIGHTNESS
3          ; AND WRITE 'SIEMENS*'
4
5          ; P3.0 = BLO\
6          ; P3.1 = BL1\
7          ; P3.2 = LT\
8          ; P3.6 = WR\
9
10         ; RO = DIGIT ADDRESS ( CHIP ENABLES – CE\ )
11         ; R1 = DIGIT COUNTER
12         ; R7 = R6 = R5 = WAIT REGISTERS
13
14         0000          .ORG 00H
15         0000          02 00 03          INIT:JMP BEGIN
16         0003          12 00 24          BEGIN:CALL WAIT1          ; DELAY FOR uC TO STABILIZE
17         0006          75 B0 00          MOV P3,#00H          ; LAMP TEST
18         0009          12 00 24          CALL WAIT1          ; DISPLAY LT\ FOR A WHILE
19         000C          75 B0 07          MOV P3,#07H          ; SET ALL 8 DISPLAYS TO 100% B
20         000F          00          NOP
21         0010          00          NOP
22         0011          78 00          MOV R0,#00H          ; DIGIT 7 ADDRESS
23         0013          79 08          MOV R1,#08H          ; 8 DIGIT COUNTER
24         0015          74 00          MOV A,#00H          ; CLEAR ACC.
25         0017          90 00 37          MOV DPTR,#TEXT          ; ADDRESS OF THE MESSAGE
26         001A          93          WRT:MOVC A,@A+DPTR          ; LOAD FIRST CHAR. INTO THE AC
27         001B          F2          MOVX @R0,A          ; DIGIT ADDRESS AND DATA WRI
28         001C          A3          INC DPTR          ; NEXT CHARACTER ADDRESS
29         001D          08          INC R0          ; NEXT DIGIT (6) ADDRESS
30         001E          E4          CLR A
31         001F          D9 F9          DJNZ R1,WRT          ; WRITE ALL 8 CHAR.
32         0021          00          GO:NOP
33         0022          01 21          JMP GO          ; MESSAGE ALWAYS ON
34         0024
35         0024
36         0024          7F 88          WAIT1:MOV R7,#88H          ; DELAY LOOPS
37         0026          00          NOP
38         0027          7E FF          WAIT2:MOV R6,#FFH
39         0029          00          NOP
40         002A          7D FF          WAIT3:MOV R5,#FFH
41         002C          00          NOP
42         002D          DD FE          DJNZ R5,$
43         002F          00          NOP
44         0030          DE F8          DJNZ R6,WAIT3
45         0032          00          NOP
46         0033          DF F2          DJNZ R7,WAIT2
47         0035          00          NOP
48         0036          22          RET
49
50         0037          53 49 45 4D 45          TEXT:DB 'SIEMENS*'
51         003C          4E 53 2A
52         003F
53         003F          .END

```